

Phase 3 Report

Luka Gobovic - 20215231

Daniel Joseph - 20217305

ELEC 374

March 24, 2023

Academic Integrity Statement

We do hereby verify that this written lab report is our own work and contains our own original ideas, concepts, and designs. No portion of this report has been copied in whole or in part from another source, with the possible exception of properly referenced material.

What Was Built Upon

The group did not add any extra functionality other than what was requested in the Phase 3 document. The only other aspect that was tweaked was that each of the instructions only ran for however many signals were present in its original control sequence. So for example, move from high only had one extra cycle after the fetch and decode. This way we avoided having extra idle cycles. Additionally, the group needed to add extra delays between each sequence to ensure that registers were correctly capturing newly updated data, and that the RAM also functioned as expected.

Simulation Waveforms

Included below are a series of ModelSim outputs for the set of instructions outlined in 3.2 of the lab procedure. The screenshots include the contents of the PC, IR, MAR, MDR, HI, LO and R0 to R15 registers, and how each are effected by each instruction can be seen. The IR shows the current instructions being executed. The figure captions below each of the images outlines which instructions are currently being displayed on the waveforms.

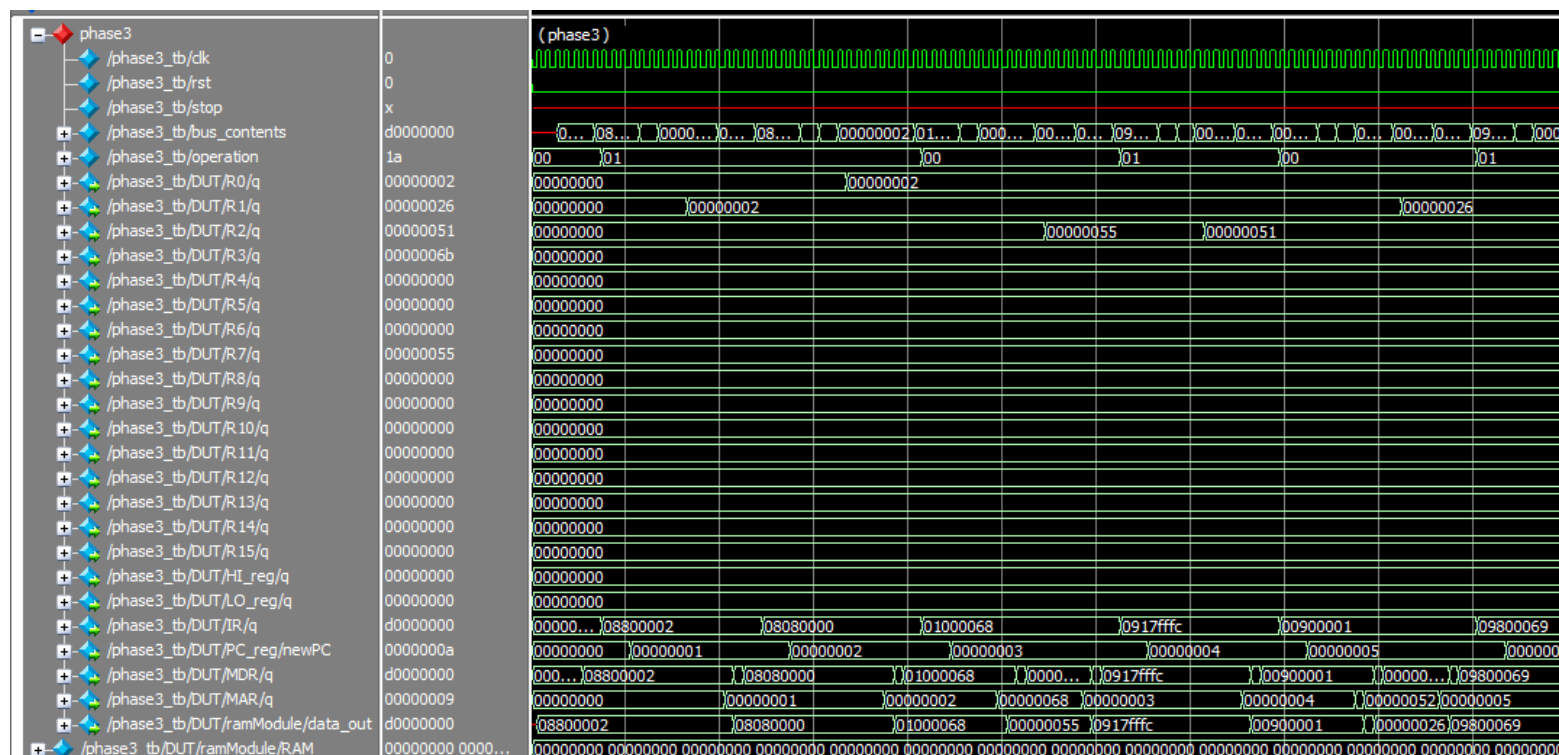


Figure 1: The waveform for instructions 1 (`ldi R1, 2`) to 5 (`ld R1, 1(R2)`).

 


Figure 2: The waveforms starting with instruction 6 (ldi R3, \$69), and ending with instruction 14 at target (add R3, R2, R3).

 


Figure 3: The waveforms for the instruction starting with `addi R7, R7, 2` to instruction 22 (`shr R2, R3, R0`).

 


Figure 4: The waveforms for instructions 22 (st \$52, R2) to instruction 30 (ldi r4, 6).

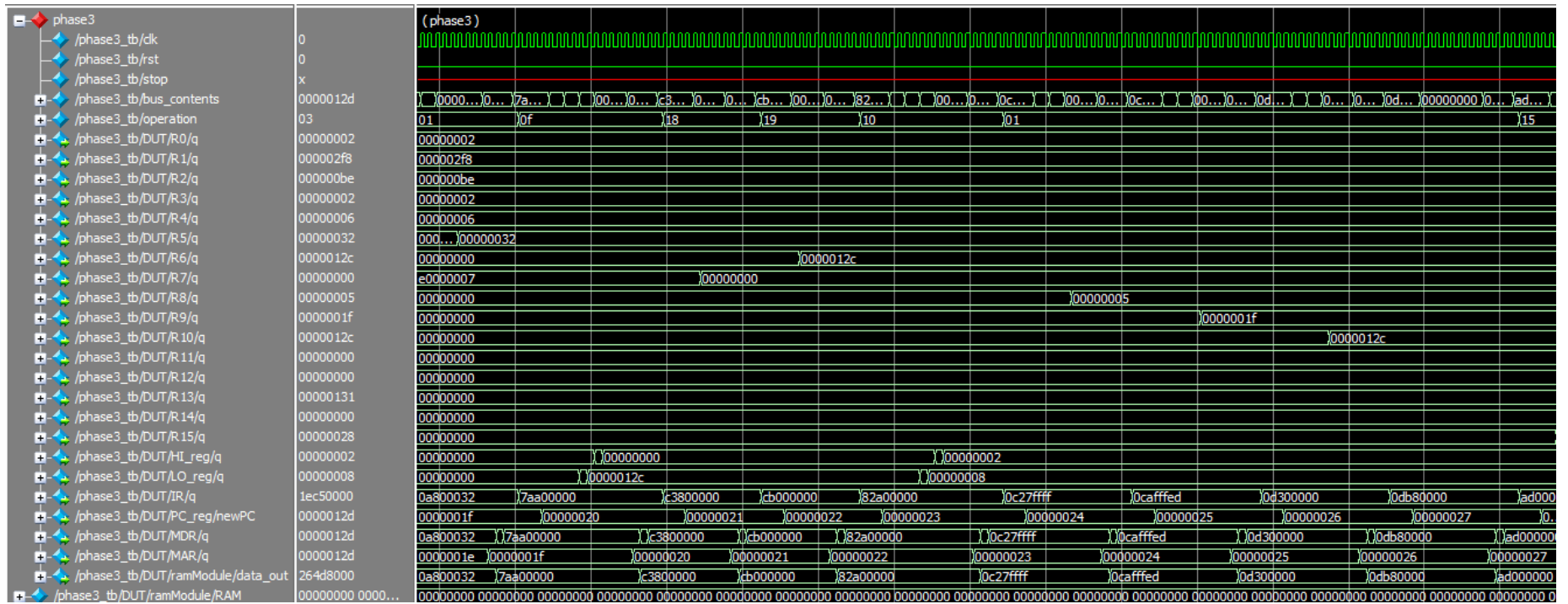


Figure 5: The waveforms for instruction 30 (ldi R5, \$32) to instruction 38 (ldi R10, 0(R6)).

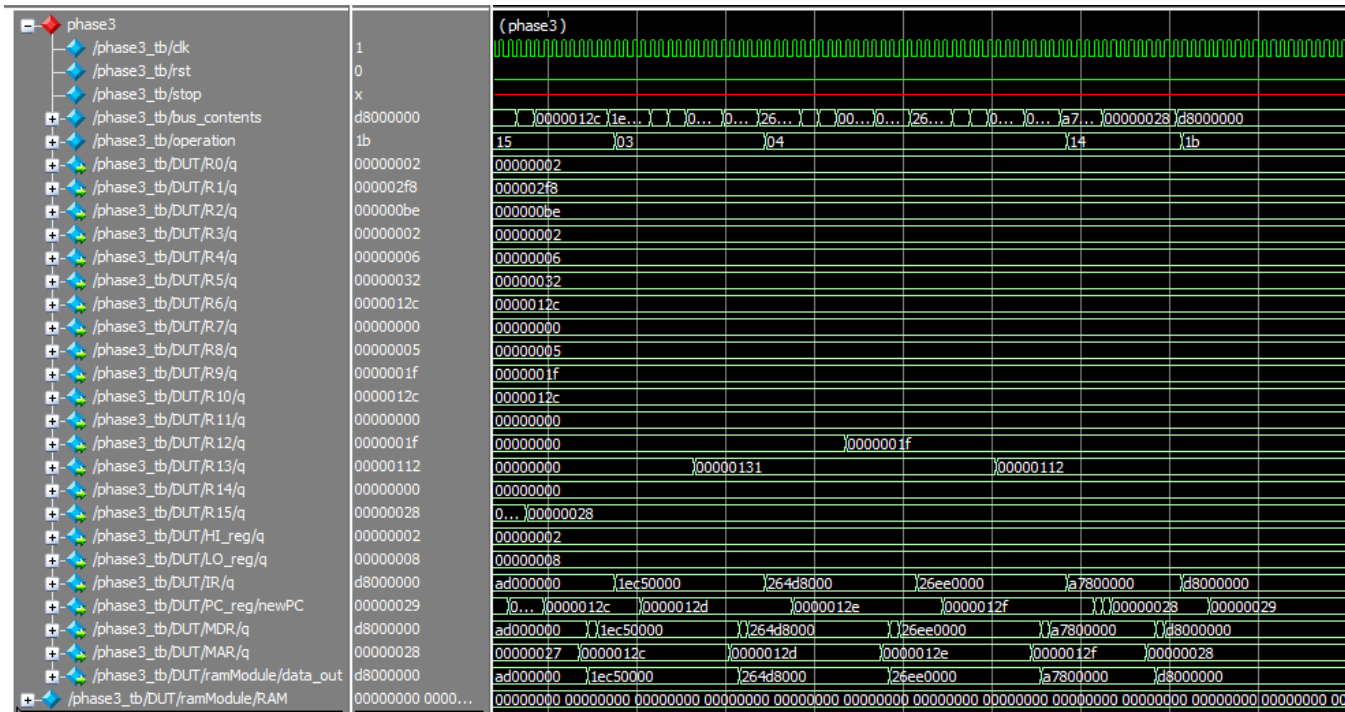


Figure 6: The waveforms for instruction 38 (*ldi R11, 0(R7)*) to the last instruction (*jr R15*). After this instruction 41 (*halt*) is executed.

RAM Contents After Execution

+	◆	[104]	000000bc	000000bc
+	◆	[103]	00000000	00000000
+	◆	[102]	00000000	00000000
+	◆	[101]	00000000	00000000
+	◆	[100]	00000000	00000000
+	◆	[99]	00000000	00000000
+	◆	[98]	00000000	00000000
+	◆	[97]	00000000	00000000
+	◆	[96]	00000000	00000000
+	◆	[95]	00000000	00000000
+	◆	[94]	00000000	00000000
+	◆	[93]	00000000	00000000
+	◆	[92]	00000000	00000000
+	◆	[91]	00000000	00000000
+	◆	[90]	00000000	00000000
+	◆	[89]	00000000	00000000
+	◆	[88]	00000000	00000000
+	◆	[87]	00000000	00000000
+	◆	[86]	00000000	00000000
+	◆	[85]	00000000	00000000
+	◆	[84]	00000000	00000000
+	◆	[83]	00000000	00000000
+	◆	[82]	0000002f	0000002f
+	◆	[81]	00000000	00000000

Locations are in decimal, so 104 would be hex \$68, 82 would be \$52, both the locations specified by the store instruction.

RAM Contents Before

1	08800002		
2	08080000		
3	01000068		
4	0917FFFC		
5	00900001		
6	09800069		
7	99980004		
8	09980002		
9	039FFFFD		
10	D0000000		
11	9B900002		
12	90000005		
13	09880002		
14	19918000	83	26
15	63B80002	84	0
16	8BB80000	85	0
17	93B80000	86	0
18	6BB8000F	87	0
19	50880000	88	0
20	7388001C	89	0
21	43B80000	90	0
22	39180000	91	0
23	11000052	92	0
24	59100000	93	0
25	31180000	94	0
26	28908000	95	0
27	11880060	96	0
28	21918000	97	0
29	48900000	98	0
30	0A000006	99	0
31	0A800032	100	0
32	7AA00000	101	0
33	C3800000	102	0
34	CB000000	103	0
35	82A00000	104	0
36	0C27FFFF	105	55
37	0CAFFFD		
38	0D300000		
39	0DB80000		
40	AD000000		
41	D8000000		

300	0
301	1EC50000
302	264D8000
303	26EE0000
304	A7800000
305	0

Verilog Code

This section only includes revised or newly added code, refer to phase 1 and 2 reports for other code.

Control Unit

```
`timescale 1ns/10ps
module control_unit (
    output reg IncPC, CONin, ramWE, MDRin, MDRout, MARin, IRin, Read, Rin, Rout, Gra, Grb, Grc,
    HIin, LOin, ZHighIn, ZLowIn, Yin, PCin, InPort_enable, OutPort_enable,
    InPortout, PCout, Yout, ZLowout, ZHighout, LOout, HIout, BAout, Cout, run,
    output reg [15:0] R_enableIn,
    input [31:0] IR,
    input clk, rst, stop
);

parameter reset_state= 8'b00000000, fetch0 = 8'b00000001, fetch1 = 8'b00000010, fetch2= 8'b00000011,
    add3 = 8'b00000100, add4= 8'b00000101, add5= 8'b00000110, sub3 = 8'b00000111, sub4 = 8'b00001000, sub5 = 8'b00001001,
    mul3 = 8'b00001010, mul4 = 8'b00001011, mul5 = 8'b00001100, mul6 = 8'b00001101, div3 = 8'b00001110, div4 = 8'b00001111,
    div5 = 8'b00010000, div6 = 8'b00010001, or3 = 8'b00010010, or4 = 8'b00010011, or5 = 8'b00010100, and3 = 8'b00010101,
    and4 = 8'b00010110, and5 = 8'b00010111, shl3 = 8'b00011000, shl4 = 8'b00011001, shl5 = 8'b00011010, shr3 = 8'b00011011,
    shr4 = 8'b00011100, shr5 = 8'b00011101, rol3 = 8'b00011110, rol4 = 8'b00011111, rol5 = 8'b00100000, ror3 = 8'b00100001,
    ror4 = 8'b00100010, ror5 = 8'b00100011, neg3 = 8'b00100100, neg4 = 8'b00100101, neg5 = 8'b00100110, not3 = 8'b00100111,
    not4 = 8'b00101000, not5 = 8'b00101001, ld3 = 8'b00101010, ld4 = 8'b00101011, ld5 = 8'b00101100, ld6 = 8'b00101101,
    ld7 = 8'b00101110, ldi3 = 8'b00101111, ldi4 = 8'b00110000, ldi5 = 8'b00110001, st3 = 8'b00110010, st4 = 8'b00110011,
    st5 = 8'b00110100, st6 = 8'b00110101, st7 = 8'b00110110, addi3 = 8'b00110111, addi4 = 8'b00111000, addi5 = 8'b00111001,
    andi3 = 8'b00111010, andi4 = 8'b00111011, andi5 = 8'b00111100, ori3 = 8'b00111101, ori4 = 8'b00111110, ori5 = 8'b00111111,
    br3 = 8'b01000000, br4 = 8'b01000001, br5 = 8'b01000010, br6 = 8'b01000011, br7 = 8'b11111111, jr3 = 8'b01000100,
    jal3 = 8'b01000101, jal4 = 8'b01000110, mfhi3 = 8'b01000111, mflo3 = 8'b01001000, in3 = 8'b01001001, out3 = 8'b01001010,
    nop3 = 8'b01001011, halt3 = 8'b01001100, fetch2a = 8'b10000000, fetch3 = 8'b11000000, shra3 = 8'b11000001,
    shra4 = 8'b11000010, shra5 = 8'b11000011;

reg [7:0] present_state = reset_state; // adjust the bit pattern based on the number of states

always @(posedge clk, posedge rst, posedge stop) // finite state machine; if clock or reset rising-
begin
    if (rst == 1'b1)
        present_state = reset_state;
    if (stop == 1'b1)
        present_state = halt3;
    else case (present_state)
        reset_state : present_state = #40 fetch0;
        fetch0 : #40 present_state = fetch1;
        fetch1 : #40 present_state = fetch2;
        fetch2 : #40 present_state = fetch2a;
        fetch2a : #40 present_state = fetch3;
        fetch3 : #20 begin
            case (IR[31:27]) // inst. decoding based on the opcode to set the next state
                5'b00011 : present_state = add3; // this is the add instruction
                5'b00100 : present_state = sub3;
                5'b00101 : present_state = and3;
                5'b00110 : present_state = or3;
                5'b01111 : present_state = mul3;
                5'b10000 : present_state = div3;
                5'b01001 : present_state = shl3;
                5'b00111 : present_state = shr3;
                5'b01000 : present_state = shra3;
                5'b01011 : present_state = rol3;
                5'b01010 : present_state = ror3;
                5'b10001 : present_state = neg3;
                5'b10010 : present_state = not3;
                5'b00000 : present_state = ld3;
                5'b00001 : present_state = ldi3;
                5'b00010 : present_state = st3;
                5'b01100 : present_state = addi3;
                5'b01101 : present_state = andi3;
                5'b01110 : present_state = ori3;
                5'b10011 : present_state = br3;
                5'b10100 : present_state = jr3;
                5'b10101 : present_state = jal3;
                5'b11000 : present_state = mfhi3;
                5'b11001 : present_state = mflo3;
                5'b10110 : present_state = in3;
                5'b10111 : present_state = out3;
            endcase
        end
    endcase
end
```

```

        5'b10111 : present_state = out3;
        5'b11010 : present_state = nop3;
        5'b11011 : present_state = halt3;
    endcase
end
add3      : #40 present_state = add4;
add4      : #40 present_state = add5;
add5      : #40 present_state = reset_state;

addi3     : #40 present_state = addi4;
addi4     : #40 present_state = addi5;
addi5     : #40 present_state = reset_state;

sub3      : #40 present_state = sub4;
sub4      : #40 present_state = sub5;
sub5      : #40 present_state = reset_state;

mul3      : #40 present_state = mul4;
mul4      : #40 present_state = mul5;
mul5      : #40 present_state = mul6;
mul6      : #40 present_state = reset_state;

div3      : #40 present_state = div4;
div4      : #40 present_state = div5;
div5      : #40 present_state = div6;
div6      : #40 present_state = reset_state;

or3       : #40 present_state = or4;
or4       : #40 present_state = or5;
or5       : #40 present_state = reset_state;

and3      : #40 present_state = and4;
and4      : #40 present_state = and5;
and5      : #40 present_state = reset_state;

shl3      : #40 present_state = shl4;
shl4      : #40 present_state = shl5;
shl5      : #40 present_state = reset_state;

shr3      : #40 present_state = shr4;
shr4      : #40 present_state = shr5;
shr5      : #40 present_state = reset_state;

shra3     : #40 present_state = shra4;
shra4     : #40 present_state = shra5;
shra5     : #40 present_state = reset_state;

rol3      : #40 present_state = rol4;
rol4      : #40 present_state = rol5;
rol5      : #40 present_state = reset_state;

ror3      : #40 present_state = ror4;
ror4      : #40 present_state = ror5;
ror5      : #40 present_state = reset_state;

neg3      : #40 present_state = neg4;
neg4      : #40 present_state = reset_state;

not3      : #40 present_state = not4;
not4      : #40 present_state = reset_state;

ld3       : #40 present_state = ld4;
ld4       : #40 present_state = ld5;
ld5       : #40 present_state = ld6;
ld6       : #40 present_state = ld7;
ld7       : #40 present_state = reset_state;

ldi3      : #40 present_state = ldi4;
ldi4      : #40 present_state = ldi5;
ldi5      : #40 present_state = reset_state;

st3       : #40 present_state = st4;
st4       : #40 present_state = st5;
st5       : #40 present_state = st6;
st6       : #40 present_state = st7;
st7       : #40 present_state = reset_state;

```

```

andi3      : #40 present_state = andi4;
andi4      : #40 present_state = andi5;
andi5      : #40 present_state = reset_state;

ori3       : #40 present_state = ori4;
ori4       : #40 present_state = ori5;
ori5       : #40 present_state = reset_state;

jal3       : #40 present_state = jal4;
jal4       : #40 present_state = reset_state;

jr3        : #40 present_state = reset_state;

br3        : #40 present_state = br4;
br4        : #40 present_state = br5;
br5        : #40 present_state = br6;
br6        : #40 present_state = br7;
br7        : #40 present_state = reset_state;

out3       : #40 present_state = reset_state;

in3        : #40 present_state = reset_state;

mflo3      : #40 present_state = reset_state;

mfhi3      : #40 present_state = reset_state;

nop3       : #40 present_state = reset_state;
always @(present_state) begin // do the job for each state
  case (present_state) // assert the required signals in each state
    reset_state: begin
      run <= 1;
      R_enableIn <= 0;
      PCout <= 0; ZLowout <= 0; MDRout <= 0;
      MARin <= 0; ZHighIn <= 0; ZLowIn <= 0; CONin<=0;
      InPort_enable<=0; OutPort_enable<=0;
      PCin <=0; MDRin <= 0; IRin <= 0;
      Yin <= 0; IncPC <= 0; ramWE <=0;
      Gra<=0; Grb<=0; Grc<=0; BAout<=0; Cout<=0;
      InPortout<=0; ZHighout<=0; LOout<=0; HIout<=0;
      HIin<=0; LOin<=0; Rout<=0; Rin<=0; Read<=0;

      end
    fetch0: begin
      #5 PCout <= 1; MARin <= 1;
    end
    fetch1: begin
      PCout <= 0; MARin <= 0; ZLowIn <= 0;
      Read <= 1; MDRin <= 1;
    end
    fetch2: begin
      ZLowout <= 0; Read <= 0; MDRin <= 0;
      #5 MDRout <= 1; IRin <= 1;
    end
    fetch2a : begin
    end
    fetch3 : begin
      MDRout <= 0; IRin <= 0;
      PCin <= 1; IncPC <= 1;
    end
  end
//END OF FETCH

```

```

//MUL AND DIVIDE
mul3, div3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rout <= 1; Yin <= 1;
end
mul4, div4: begin
    Gra <= 0; Rout <= 0; Yin <= 0;
    Grb <= 1; Rout <= 1; ZLowIn <= 1; ZHighIn <= 1;
end
mul5, div5: begin
    Grb <= 0; Rout <= 0; ZLowIn <= 0; ZHighIn <= 0;
    ZLowout <= 1; LOin <= 1;
end
mul6, div6: begin
    ZLowout <= 0; LOin <= 0;
    ZHighout <= 1; HIin <= 1;
    // #40 Zhighout <= 0; HIin <= 0;
end
//Intermediate Inst
andi3, ori3, addi3: begin
    PCin <= 0; IncPC <= 0;
    Grb <= 1; Rout <= 1; Yin <= 1;
end
andi4, ori4, addi4: begin
    Grb <= 0; Rout <= 0; Yin <= 0;
    Cout <= 1; ZHighIn <= 1; ZLowIn <= 1;
end
andi5, ori5, addi5: begin
    Cout <= 0; ZHighIn <= 0; ZLowIn <= 0;
    ZLowout <= 1; Gra <= 1; Rin <= 1;
    // #40 ZLowout <= 0; Gra <= 0; Rin <= 0;
end

//Not Neg
not3, neg3: begin
    PCin <= 0; IncPC <= 0;
    Grb <= 1; Rout <= 1; ZLowIn <= 1;
end
not4, neg4: begin
    Grb <= 0; Rout <= 0; ZLowIn <= 10;
    ZLowout <= 1; Gra <= 1; Rin <= 1;
end
//LOAD
ld3: begin
    PCin <= 0; IncPC <= 0;
    Grb <= 1; BAout <= 1; Yin <= 1;
end
ld4: begin
    Grb <= 0; BAout <= 0; Yin <= 0;
    Cout <= 1; ZHighIn <= 1; ZLowIn <= 1;
end
ld5: begin
    Cout <= 0; ZHighIn <= 0; ZLowIn <= 0;
    ZLowout <= 1; MARin <= 1;
end
ld6: begin
    ZLowout <= 0; MARin <= 0;
    Read <= 1; MDRin <= 1;
end
ld7: begin
    Read <= 0; MDRin <= 0;
    MDRout <= 1; Gra <= 1; Rin <= 1;
    // #40 MDRout <= 0; Gra <= 0; Rin <= 0;
end

```

```

//Load Intermediate
ldi3: begin
    PCin <= 0; IncPC <= 0;
    Grb <= 1; BAout <= 1; Yin <= 1;
end
ldi4: begin
    Grb <= 0; BAout <= 0; Yin <= 0;
    Cout <= 1; ZHighIn <= 1; ZLowIn <= 1;
end
ldi5: begin
    Cout <= 0; ZHighIn <= 0; ZLowIn <= 0;
    ZLowout<= 1; Gra <= 1; Rin <= 1;
end
//Store
st3: begin
    PCin <= 0; IncPC <= 0;
    Grb <= 1; BAout <= 1; Yin <= 1;
end
st4: begin
    Grb <= 0; BAout <= 0; Yin <= 0;
    Cout <= 1; ZHighIn <= 1; ZLowIn <= 1;
end
st5: begin
    Cout <= 0; ZHighIn <= 0; ZLowIn <= 0;
    ZLowout<= 1; MARin <= 1;
end
st6: begin
    ZLowout<= 0; MARin <= 0;
    Read <= 0; Gra <= 1; Rout <= 1; MDRin <= 1;
end
st7: begin
    Gra <= 0; Rout <= 0; MDRin <= 0; MDRout <= 1;
    ramWE <= 1;
end

//Jump
jr3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rout <= 1; PCin <= 1;
end
//Jump and Link
jal3: begin
    PCin <= 0; IncPC <= 0;
    PCout <= 1; R_enableIn <= 16'h8000;
end
jal4: begin
    PCout <= 0; R_enableIn <= 16'h0;
    Gra <= 1; Rout <= 1; PCin <= 1;
end
//Outport
out3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rout <= 1; OutPort_enable <= 1;
end
//Inport
in3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rin <= 1; InPortout <= 1;
end
//Move from HI
mfhi3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rin <= 1; HIout <= 1;
end
//Move from LO
mflo3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rin <= 1; LOout <= 1;
end

```

```

//Branch
br3: begin
    PCin <= 0; IncPC <= 0;
    Gra <= 1; Rout <= 1; CONin <= 1;
end
br4: begin
    Gra <= 0; Rout <= 0; CONin <= 0;
    PCout <= 1; Yin <= 1;
end
br5: begin
    PCout <= 0; Yin <= 0;
    Cout <= 1; ZLowIn <= 1; ZHighIn <= 1;
end
br6: begin
    Cout <= 0; ZLowIn <= 0; ZHighIn <= 0;
    ZLowout <= 1; PCin <= 1;
end
br7: begin
    ZLowout <= 0; PCin <= 0;
    PCout <= 1; MARin <= 1;
end
//No OP
nop3 : begin
    PCin <= 0; IncPC <= 0;
end
//Halt
halt3: begin
    PCin <= 0; IncPC <= 0;
    run <= 0;
end

```


Datapath

```
module CPUDesignProject(
    input clk, rst, stop,
    input wire [31:0] inport_data_in,
    output wire [31:0] outport_data_out, bus_contents,
    output [4:0] operation
);

    wire IncPC, CONin, ramWE, MDRin, MDRout, MARin, IRin, Read, R_in, R_out, Gra, Grb, Grc,
    HIin, LOin, ZHighIn, ZLowIn, Yin, PCin, InPort_enable, OutPort_enable,
    InPortout, PCout, ZLowout, ZHighout, LOout, HIout, BAout, Cout, Run;

    reg [15:0] regEnable; //which register is enabled
    reg [15:0] regOut; //Which register to output

    wire [15:0] regEnable_IR, regEnable_In, Rout_IR;

    //reg [15:0] regIn;

    initial begin
        regEnable = 16'b0;
        regOut = 16'b0;
    end

    //Chooses which registers enable signal is asserted, and which output signal is asserted (placed on bus)
    always@(*)begin
        if (regEnable_IR)
            regEnable <= regEnable_IR;
        else
            regEnable <= regEnable_In;

        if (Rout_IR)
            regOut <= Rout_IR;
        else
            regOut <= 16'b0;
    end

    //These are the inputs to the bus multiplexer
    wire [31:0] R0_data_out, R1_data_out, R2_data_out, R3_data_out, R4_data_out, R5_data_out, R6_data_out, R7_data_out, R8_data_out, R9_data_out;
    wire [31:0] R10_data_out, R11_data_out, R12_data_out, R13_data_out, R14_data_out, R15_data_out, HI_data_out, LO_data_out;
    wire [31:0] ZHigh_data_out, ZLow_data_out, IR_data_out;
    wire [31:0] PC_data_out, MDR_data_out, RAM_data_out, MAR_data_out_32, C_Sign_extend, Y_data_out, pcData;
    wire [63:0] C_data_out;
    wire [8:0] MAR_data_out;

    // Encoder input and output wires
    wire [31:0] encoder_in;
    wire [4:0] encoder_out;

    // Connecting the register output signals to the encoder's input wire
    assign encoder_in = {{8{1'b0}}, Cout, InPortout, MDRout, PCout, ZLowout, ZHighout, LOout, HIout, regOut};

    // Instatiating 32-to-5 encoder
    encoder_32_to_5 encoder(encoder_in, encoder_out);

    //Creating all 32-bit registers
    wire [31:0] r0_out;
    reg_32_bit R0(clk, clr, regEnable[0], bus_contents, r0_out);
    assign R0_data_out = {32{!BAout}} & r0_out; //revision to R0
```

```

//Registers
reg_32_bit R1(clk, clr, regEnable[1], bus_contents, R1_data_out);
reg_32_bit R2(clk, clr, regEnable[2], bus_contents, R2_data_out);
reg_32_bit R3(clk, clr, regEnable[3], bus_contents, R3_data_out);
reg_32_bit R4(clk, clr, regEnable[4], bus_contents, R4_data_out);
reg_32_bit R5(clk, clr, regEnable[5], bus_contents, R5_data_out);
reg_32_bit R6(clk, clr, regEnable[6], bus_contents, R6_data_out);
reg_32_bit R7(clk, clr, regEnable[7], bus_contents, R7_data_out);
reg_32_bit R8(clk, clr, regEnable[8], bus_contents, R8_data_out);
reg_32_bit R9(clk, clr, regEnable[9], bus_contents, R9_data_out);
reg_32_bit R10(clk, clr, regEnable[10], bus_contents, R10_data_out);
reg_32_bit R11(clk, clr, regEnable[11], bus_contents, R11_data_out);
reg_32_bit R12(clk, clr, regEnable[12], bus_contents, R12_data_out);
reg_32_bit R13(clk, clr, regEnable[13], bus_contents, R13_data_out);
reg_32_bit R14(clk, clr, regEnable[14], bus_contents, R14_data_out);
reg_32_bit R15(clk, clr, regEnable[15], bus_contents, R15_data_out);
reg_32_bit Y(clk, clr, Yin, bus_contents, Y_data_out);
reg_32_bit HI_reg(clk, clr, HIin, bus_contents, HI_data_out);
reg_32_bit LO_reg(clk, clr, LOin, bus_contents, LO_data_out);
reg_32_bit ZHigh_reg(clk, clr, ZHighIn, C_data_out[63:32], ZHigh_data_out);
reg_32_bit ZLow_reg(clk, clr, ZLowIn, C_data_out[31:0], ZLow_data_out);

reg_32_bit IR(clk, rst, IRin, bus_contents, IR_data_out);

IncPC_32_bit PC_reg(clk, IncPC, PCin, bus_contents, PC_data_out);

reg_32_bit OutPort(clk, clr, OutPortIn, bus_contents, outport_data_out);
reg_32_bit InPort(clk, clr, InPortIn, Inport_data_out, BusMuxIn_In_Port);

//Select and encode Logic and CON FF
selectencodelogic selEn(IR_data_out, Gra, Grb, Grc, R_in, R_out, BAout, C_Sign_extend,
    regEnable_IR, Rout_IR, operation);
CONFF_logic conff(IR_data_out[20:19], bus_contents, CONin, CONout);

//MDR
wire [31:0] MDR_mux_out;
//First create the 2-1 mux that selects either the RAM or the bus contents
mux_2_to_1 MDMux(bus_contents, RAM_data_out, Read, MDR_mux_out);
//Create the actual MDR itself by instantiating a regular 32 bit reg
reg_32_bit MDR(clk, rst, MDRin, MDR_mux_out, MDR_data_out);

//This is done to avoid having to make an MAR unit module
reg_32_bit MAR(clk, rst, MARin, bus_contents, MAR_data_out_32);
assign MAR_data_out = MAR_data_out_32[8:0];

//memRAM ramModule(MAR_data_out, clk, MDR_data_out, Read, ramWE, RAM_data_out);
ram ramModule(MDR_data_out, MAR_data_out, clk, ramWE, RAM_data_out);

// Multiplexer to select which data to send out on the bus
mux_32_to_1 BusMux(
    .BusMuxIn_R0(R0_data_out), .BusMuxIn_R1(R1_data_out), .BusMuxIn_R2(R2_data_out), .BusMuxIn_R3(R3_data_out),
    .BusMuxIn_R4(R4_data_out), .BusMuxIn_R5(R5_data_out), .BusMuxIn_R6(R6_data_out), .BusMuxIn_R7(R7_data_out),
    .BusMuxIn_R8(R8_data_out), .BusMuxIn_R9(R9_data_out), .BusMuxIn_R10(R10_data_out), .BusMuxIn_R11(R11_data_out),
    .BusMuxIn_R12(R12_data_out), .BusMuxIn_R13(R13_data_out), .BusMuxIn_R14(R14_data_out), .BusMuxIn_R15(R15_data_out),
    .BusMuxIn_HI(HI_data_out), .BusMuxIn_LO(LO_data_out), .BusMuxIn_Z_HI(ZHigh_data_out), .BusMuxIn_Z_LO(ZLow_data_out),
    .BusMuxIn_PC(PC_data_out), .BusMuxIn_MDR(MDR_data_out), .BusMuxIn_In_Port(Inport_data_out), .C_Sign_Extended(C_Sign_extend),
    .BusMuxOut(bus_contents), .select(encoder_out)
);

```

```

        control_unit controlUnit(
            .PCout(PCout),
            .ZHighout(ZHighout),
            .ZLowout(ZLowout),
            .MDRout(MDRout),
            .MARin(MARin),
            .PCin(PCin),
            .MDRin(MDRin),
            .IRin(IRin),
            .Yin(Yin),
            .IncPC(IncPC),
            .Read(Read),
            .HIin(HIin),
            .LOin(LOin),
            .HIout(HIout),
            .LOout(LOout),
            .ZHighIn(ZHighIn),
            .ZLowIn(ZLowIn),
            .Cout(Cout),
            .ramWE(ramWE),
            .Gra(Gra),
            .Grb(Grb),
            .Grc(Grc),
            .Rin(R_in),
            .Rout(R_out),
            .BAout(BAout),
            .CONin(CONin),
            .InPort_enable(InPortIn),
            .OutPort_enable(OutPortIn),
            .InPortout(InPortout),
            .run(Run),
            .R_enableIn(regEnable_In),
            .IR(IR_data_out),
            .clk(clk),
            .rst(rst),
            .stop(stop)
        );

//instantiate the alu
alu the_alu(
    .clk(clk),
    .clr(rst),
    .branch_flag(CONout),
    .A(Y_data_out),
    .B(bus_contents),
    .opcode(operation),
    .C(C_data_out)
);

```

Increment PC

```

module IncPC_32_bit #(parameter qInitial = 0) (
    input clk, IncPC, enable,
    input [31:0] curPC,
    output reg[31:0] newPC
);

initial newPC = qInitial;

always @ (posedge clk)
begin
    if(IncPC == 1 && enable == 1)
        newPC <= newPC + 1;
    else if (enable == 1)
        newPC <= curPC;
    end
endmodule

```